

Logic Gates / පද්ධති

Basic logic gate


- * AND
- * OR
- * NOT

Combinational

- * NAND
- * XOR
- * NOR
- * XNOR

Basic Logic Gates

AND gate - [සමතුලිත]

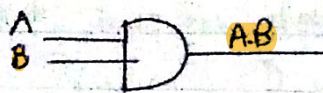


Truth table -
සමතුලිත පද්ධති

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

* AND operator produces a logical True only when both inputs are logical true.

OR Gate - [එකතු]

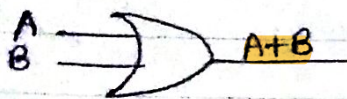

* OR operator produces a logical true output when any of input is logical True.

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

NOT Gate [වෙනස්]



A	$\bar{A}$
0	1
1	0

Combination Gates

NAND Gate

NOT + AND $\rightarrow$ NAND



A	B	AB	$\overline{AB}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

* NOT operator $\Rightarrow$ Perform a simple inverse

NOR Gate

NOT + OR

→ NOR



A	B	$A+B$	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

* NOR is equivalent to an OR operation followed by a NOT operation

XOR Gate



$$\Rightarrow \{ \oplus \Rightarrow A\bar{B} + \bar{A}B \}$$


* XOR produces a logical true when either of its inputs is logical true.

A	B	$A+B$	$A\oplus B$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

* ଯଦିଦୁଇ ଇନପୁଟ୍ ଉଭୟ output "0" ଚାହୁଁନ୍ତି.
* ଯଦିଦୁଇ ଇନପୁଟ୍ କେବଳ ଗୋଟିଏ output "1" ଚାହୁଁନ୍ତି.

XNOR Gate

XOR + NOT → XNOR

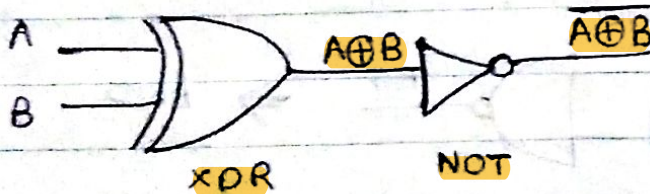

A	B	$A\oplus B$	$\overline{A\oplus B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

NAND } universal gate
NOR }

சிந்தனை மூலம்

 $\overline{AB}$



NAND $\rightarrow$

A	B	$\overline{A}B$	$A\overline{B}$
0	0	0	1
0	1	0	1
1	0	1	0
1	1	0	0

NOT ജ്ഞാതാവ

 $\Rightarrow$ NAND $\rightarrow$ NOT

NAND $\rightarrow$ AND
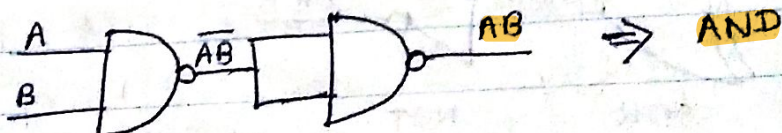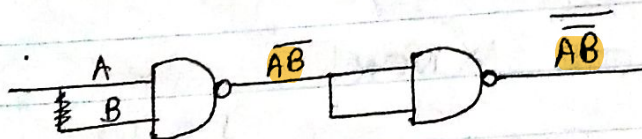
$$\overline{A \cdot B} \longrightarrow AB$$
$$\overline{\overline{AB}} \Rightarrow AB$$


NAND $\longrightarrow$ OR


$$\overline{AB} \longrightarrow A+B$$

$$\left. \begin{aligned} \overline{A \cdot B} &= \overline{A} + \overline{B} \\ \overline{A + B} &= \overline{A} \cdot \overline{B} \end{aligned} \right\} \rightarrow$$

$$\overline{AB} \Rightarrow \overline{A+B} \rightarrow A+B$$

$$\Rightarrow \overline{\overline{A+B}} = A+B //$$
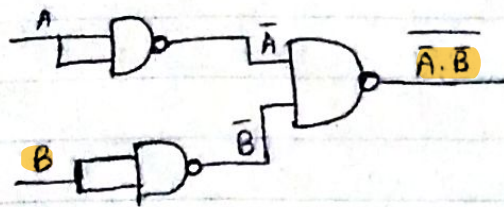
$$A+B = \overline{\overline{A+B}} = \overline{AB}$$




$$NOR \rightarrow AND$$

$$\overline{A+B} \rightarrow AB$$

$$\overline{A+B} = \overline{A} \cdot \overline{B} = AB$$

$$\overline{AB} = AB$$

$$\overline{A+B} = AB$$

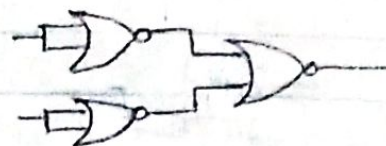



Universal Gate Short notes

	NOT	AND	OR
NAND			
NOR			

Truth Table Short notes.

A	B	AND	OR	NAND	NOR	XXOR XNOR	XXOR XOR
0	0	0	0	1	1	1	0
1	0	0	1	1	0	0	1
0	1	0	1	1	0	0	1
1	1	1	1	0	0	1	0

① $F = \bar{C} + A\bar{B}$

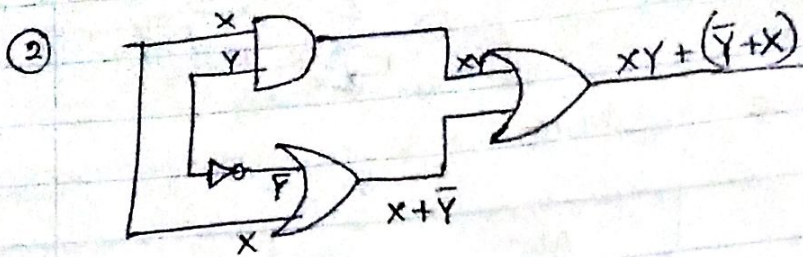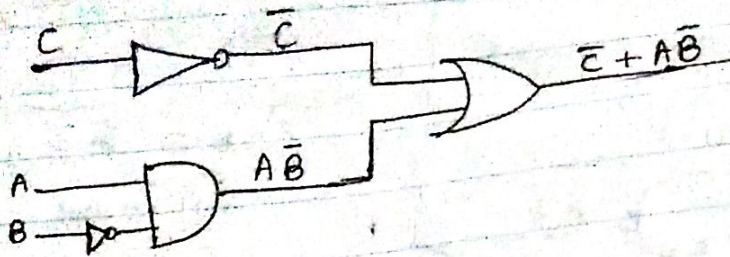

Booleans laws

Law of sum

- ① $A + 1 = 1$
- ② $A + A = A$
- ③ $A + 0 = A$
- ④ $A + \bar{A} = 1$

* $A \oplus B = A\bar{B} + \bar{A}B$

Law of product

- ⑤ $A \times 1 = A$
- ⑥ $A \times A = A$
- ⑦ $A \times 0 = 0$
- ⑧ $A \times \bar{A} = 0$

De morgan's Law

- ⑨ $\overline{A+B} = \bar{A} \cdot \bar{B}$
- ⑩ $\overline{A \cdot B} = \bar{A} + \bar{B}$

Redundancy law

- ⑪ $X + \bar{X}Y = X + Y$
 $X + \bar{X}Y = (X + \bar{X}) \cdot (X + Y)$

$A \times A = A$

$A \times A \times A = A$

$A + A + A = A$

Distribution Law

* $A + BC = (A+B) \cdot (A+C)$

$$\begin{aligned} \textcircled{1} \quad & AB + A\bar{B} \\ & A(B + \bar{B}) \\ & A \times 1 \\ & = A \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad & (A+B)(A+\bar{B}) \\ & A + B\bar{B} \\ & A + 0 \\ & = A \end{aligned}$$

$$\begin{aligned} & A \cdot A + A\bar{B} + BA + B\bar{B} \\ & A + A\bar{B} + AB + 0 \\ & A + A(\bar{B} + B) \\ & A + A \times 1 = A \end{aligned}$$

$$\textcircled{3} \quad (\overline{A \cdot BC})(A + BC)$$

$$(\bar{A} + \overline{BC})(A + BC)$$

$$(\bar{A} + BC)(A + BC)$$

$$BC + A \cdot \bar{A}$$

$$BC + 0$$

$$BC$$

$$\textcircled{4} \quad \bar{A}(A+B) + (B + \overline{A \cdot A})(\bar{A} + \bar{B})$$

$$\bar{A} \cdot A + B\bar{A} + (B + \bar{A})(\bar{A} + \bar{B})$$

$$0 + B\bar{A} + (B + \bar{A})(\bar{A} + \bar{B})$$

$$B\bar{A} + B\bar{A} + B\bar{B} + \bar{A}\bar{A} + \bar{A}\bar{B}$$

$$B\bar{A} + B\bar{A} + 0 + 0 + \bar{A}\bar{B}$$

$$\textcircled{5} \quad (\overline{A+B})(\overline{A+B})$$

$$(\overline{A+B}) + (\overline{A+B})$$

$$\bar{A} + \bar{B} + \bar{A} + \bar{B}$$

$$\bar{A} + \bar{B} + \bar{A} + \bar{B}$$

$$\bar{A} + \bar{B} + A + B$$

$$B(\bar{A} + 1) + A$$

$$B + A$$

$$\textcircled{6} \quad ABC + A\bar{B}C + ABC$$

$$= AC(B + \bar{B}) + ABC$$

$$= AC(1) + ABC$$

$$= A(C + BC)$$

$$= A(C + B)$$

$$= AC + AB$$

$$\textcircled{7} \quad (\overline{A+B})(\overline{A+B})$$

$$(\bar{A} + \bar{B}) + (\bar{A} + \bar{B})$$

$$\bar{A} + \bar{B} + \bar{A} + \bar{B}$$

$$\bar{A} + \bar{B} + \bar{A} + \bar{B}$$

$$\bar{A}(\bar{B} + B)$$

$$\bar{A} \times 1$$

$$\bar{A}$$


$$\textcircled{7} \quad ABC + A\bar{B}C + AB\bar{C} + \bar{A}BC$$

$$AB(C + \bar{C}) + AC(\bar{B} + B)$$

$$AB(1) + AC(1)$$

$$AB + AC$$

$$A(B + C) = AB + AC$$

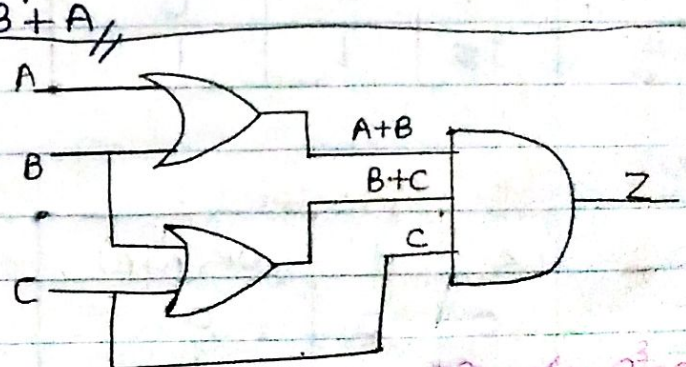


എല്ലാ വാറും 3

3 വാറും = $2^3 = 8$


$$Z = (A+B)(B+C) \cdot C$$

Truth table $\Rightarrow$

A	B	C	A+B	B+C	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	1	1	1
1	1	1	1	1	1

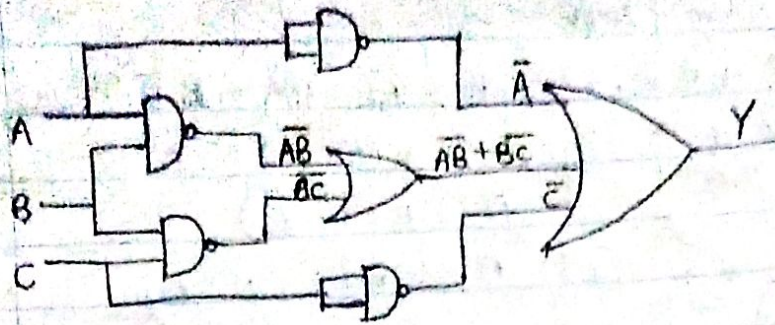
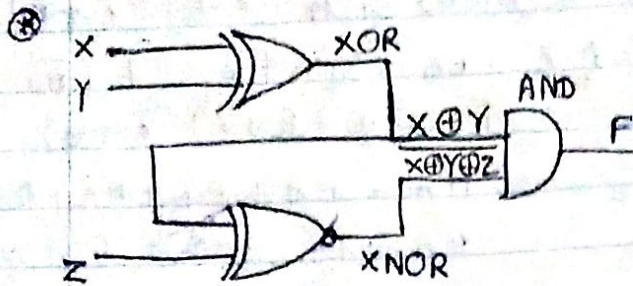
$$Y = \bar{A} + \bar{A}B + \bar{B}C + \dots$$



$$F = (X \oplus Y) \cdot (X \oplus Y \oplus Z)$$

$$F = (X \oplus Y) \cdot (\overline{X \oplus Y} \oplus Z)$$

$$F = (X \oplus Y) \cdot ((\overline{X \oplus Y}) \cdot Z)$$

Logical Operators

AND Operator

A	B	AND (A · B)
0	0	0
0	1	0
1	0	0
1	1	1

NAND operator

A	B	NAND ($\overline{A \cdot B}$)
0	0	1
0	1	1
1	0	1
1	1	0

OR operator

A	B	OR (A + B)
0	0	0
0	1	1
1	0	1
1	1	1

NOR operator

A	B	NOR ($\overline{A + B}$)
0	0	1
0	1	0
1	0	0
1	1	0

NOT operator

A	($\bar{A}$) NOT
0	1
1	0

XOR (Exclusive-OR) operator

A	B	XOR (A ⊕ B)
0	0	0
0	1	1
1	0	1
1	1	0

0 1
 ഉപയോഗിക്കുക
 കലർത്തുക
 കലർത്തുക
 കലർത്തുക
 കലർത്തുക
 XOR

Logical Function.

$$\begin{aligned}
 \textcircled{1} \quad & AB + A\bar{B}C + A\bar{B}\bar{C} \\
 &= AB + A\bar{B}(C + \bar{C}) \\
 &= A(AB) + A\bar{B} \cdot 1 \\
 &= AB + A\bar{B} \\
 &= A(\underbrace{B + \bar{B}}_1) \\
 &= A //
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{2} \quad & A + \bar{A}B \\
 &= (A + \bar{A}) \cdot (A + B) \\
 &= 1 \cdot (A + B) \\
 &= A + B //
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{3} \quad & A + \bar{A}\bar{B} \\
 &= (A + \bar{A})(A + \bar{B}) \\
 &= 1 \cdot (A + \bar{B}) \\
 &= (A + \bar{B}) //
 \end{aligned}$$


$$\begin{aligned}
 \textcircled{4} \quad & \bar{A} + AB \\
 &= (\bar{A} + A) \cdot (\bar{A} + B) \\
 &= 1 \cdot (\bar{A} + B) \\
 &= (\bar{A} + B) //
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{5} \quad & A\bar{B} + AB + \bar{A}B \\
 &= A(\bar{B} + B) + \bar{A}B \\
 &= A \times 1 + \bar{A}B \\
 &= A + \bar{A}B \\
 &= (\underbrace{A + \bar{A}}_1) \cdot (A + B) \\
 &= A + B //
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{6} \quad & A\bar{B} + AB + \bar{A}B + AB \\
 &= A(\bar{B} + B) + B(\bar{A} + A) \\
 &= A \times 1 + B \times 1 \\
 &= A + B //
 \end{aligned}$$



⑦ Design $f(A, B, C)$
 $= A + \bar{B}C$

Using Basic Logic gate.

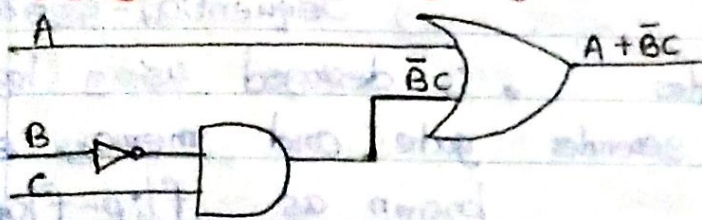


$$\begin{aligned}
 & \bar{A} \cdot B\bar{C} \\
 & \bar{A} + \bar{B}\bar{C} \\
 &= A + \bar{B}C //
 \end{aligned}$$

Using universal Logic gate.

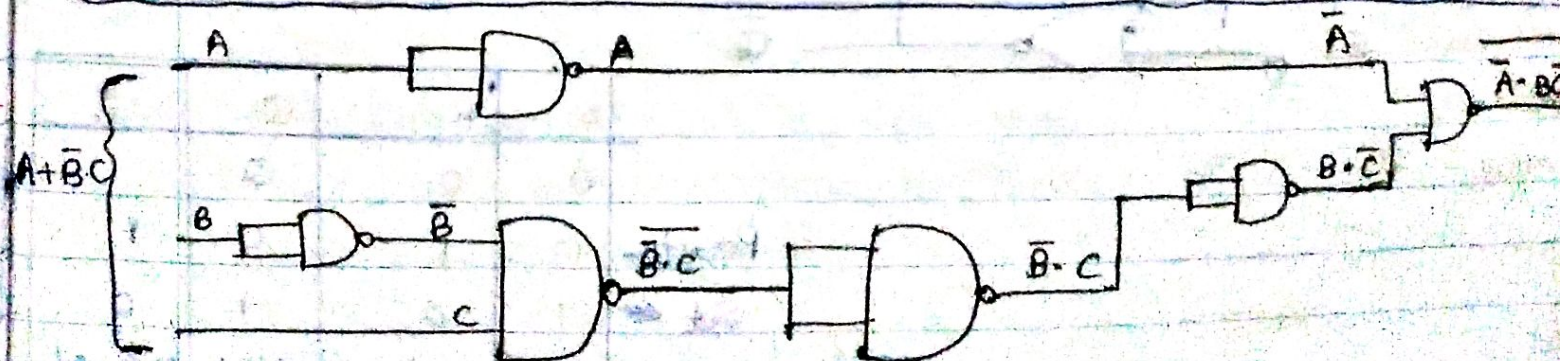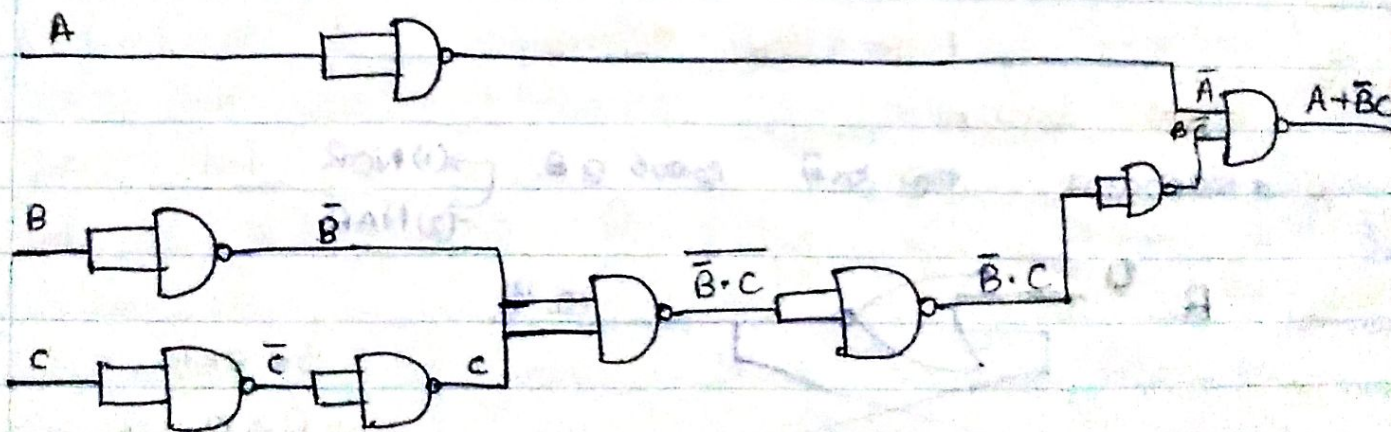

Combinational Logic circuit

2=1

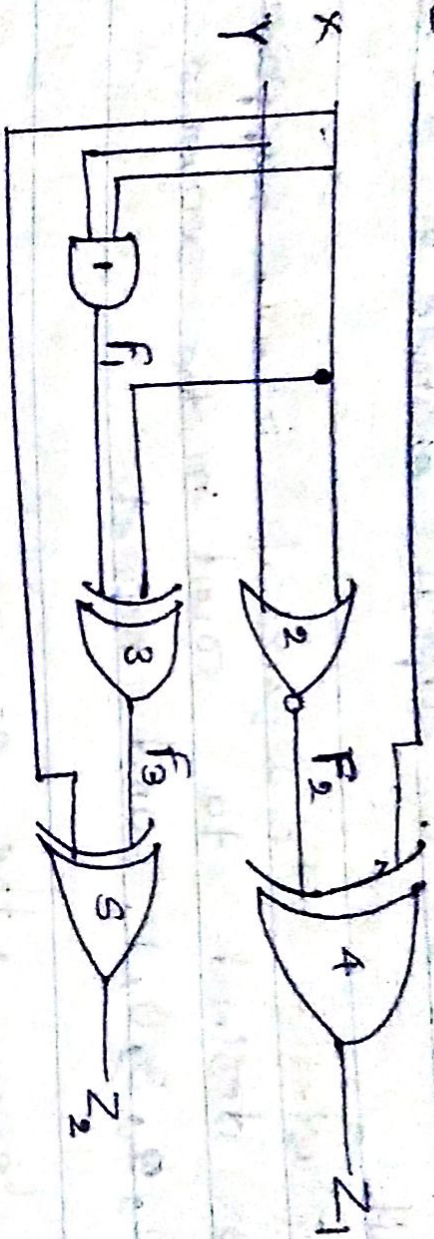

input $\Rightarrow X, Y, Z$

Output $\Rightarrow Z_1, Z_2$

$$F_1 = X_3 Y$$

$$F_2 = X + Y$$

$$Z_1 = 1 \oplus F_2$$

$$Z_1 = 1 \oplus X + Y$$

$$F_3 = X \oplus XY$$

$$Z_2 = F_3 \oplus X$$

$$Z_2 = (X \oplus XY) \oplus X$$

$$Z_2 = X \oplus (X(1 \oplus Y))$$

$$= X \oplus XY$$

$$= \text{Since } 1 \oplus Y = \bar{Y}$$

$$= X(1 \oplus \bar{Y})$$

$$Z_2 = XY \text{ Since } 1 + \bar{Y} = Y$$

$$Z_2 = X \oplus (X \oplus XY) = X \oplus X \oplus XY$$

$$= 0 \oplus XY = XY$$

Design of a combination circuit

Truth table:

Input		Output	
X	Y	Z ₁	Z ₂
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Operator

① Arithmetics

- Addition
- Subtraction
- Multiplication
- Division

② Comparison

- < less than
- > Greater than
- ≤ less than or equal
- ≥ Greater than or equal
- = equal
- ≠ not equal

③ Logic

- ~~AND~~ AND
- OR
- NOT
- NOR
- NAND
- X-OR
- ~~X-OR~~ X-NOR

1-bit addition

$$\begin{aligned}
 0 + 0 &= 0 \\
 0 + 1 &= 1 \\
 1 + 0 &= 1 \\
 1 + 1 &= 0
 \end{aligned}$$

1-bit Subtraction

$$\begin{aligned}
 0 - 0 &= 0 \\
 0 - 1 &= 1 \\
 1 - 0 &= 1 \\
 1 - 1 &= 0
 \end{aligned}$$

⊛ XOR ← both 1-bit addition and 1-bit Subtraction

Logic function

① What is function?

Relationship between two variables.

a, b, c ⇒ logic variable

$$f(a, b, c) = abc + \bar{a}b\bar{c} \rightarrow \text{logic function}$$

Logic function $\xrightarrow{\text{Domain}}$ 0, 1

Simplify following boolean expression.

$$\textcircled{1} A(\bar{A}+B) \cdot C = A \cdot \underbrace{\bar{A}}_0 C + A \cdot BC = \underbrace{0}_{\psi} + ABC = ABC //$$

$$\begin{aligned} \textcircled{2} \bar{A}\bar{B} \cdot (A+B) &= \bar{A}\bar{B}A + \bar{A}\bar{B}B \\ &= \underbrace{\bar{A}A}_{\psi} + \bar{A}\bar{B} + \bar{B}A + \underbrace{\bar{B}B}_{\psi} \\ &= \bar{A}\bar{B} + \bar{B}A // = (A \oplus B) \end{aligned}$$

$$\textcircled{3} \overline{(A+B)} + \bar{B}C = \bar{A}\bar{B} + \bar{B}C = \bar{B}(\bar{A}+C) //$$

$$\begin{aligned} \textcircled{4} x \cdot y (x+y) + x &= xy \cdot x + x \cdot y \cdot y + x \\ &= xy + xy + x \\ &= xy + x \\ &= x(\underbrace{y+1}_1) = x // \end{aligned}$$

$$\begin{aligned} \textcircled{5} \bar{p} + \bar{p}(q+x) + xq &= \bar{p} + \bar{p}q + \bar{p}x + xq \\ &= \bar{p}(1+q) + x(\bar{p}+q) \\ &= \bar{p} + \bar{p}x + xq \\ &= \bar{p}(1+x) + xq \\ &= \bar{p} + \underbrace{xq}_{\psi} // \end{aligned}$$

$$\textcircled{6} \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$

$$= \bar{A}\bar{B}(\bar{C}D + C\bar{D}) + A\bar{B}\bar{D}(\bar{C}+C)$$

$$= \bar{A}\bar{B} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{D}$$

$$= \bar{B}(\bar{A}\bar{C}D + \bar{A}C\bar{D} + A\bar{D})$$

$$= \bar{B}(\bar{A}\bar{C}D + \bar{D}(\bar{A}C + A))$$

$$= \bar{B}(\bar{A}\bar{C}D + \bar{D}(A+\bar{A})(A+C))$$

$$= \bar{B}(\bar{A}\bar{C}D + \bar{D}A + \bar{D}C) //$$

Karnaugh Map (K-Map)

Input 2 bit A, B

A	B	F
0	1	0
1	0	1
0	0	1
1	1	0

↑ 4 cells
k-Map ഉപയോഗിച്ച്

K-Map

Origin 2 bit

Origin 2 bit ഉപയോഗിച്ച് → 4 cells '0' ഉണ്ട്

B A

0	1	1
1		

* കരുതുക k-map ഉപയോഗിച്ച്

(1) Boolean ഉത്തരങ്ങൾ ക്രമം നൽകുക.

• Output ഉപയോഗിച്ച് 1 ഉപയോഗിച്ച്
Boolean ഉത്തരങ്ങൾ കാഴ്ച

$$F = A \cdot B + \bar{A} \cdot \bar{B}$$

ഈ k-map ഉപയോഗിച്ച്

K-Map Group നിർമ്മാണം

① 4 ഉപയോഗിച്ച് 1 ഉപയോഗിച്ച് 2 ഉപയോഗിച്ച് 2 ഉപയോഗിച്ച്

01	11	10	00
1	1	1	1
1	0	1	0

1	0	0	0
0	1	0	0
1	0	1	0
0	0	0	1
1	0	0	1
0	1	0	1
0	1	0	1
0	1	0	1

① $F = \bar{A}B + AB$

B \ A	0	1
0	0	0
1	1	1

$$F = B(\bar{A} + A)$$

$$= B \cdot 1$$

$$F = B //$$

② $F = \bar{A}\bar{B} + \bar{A}B + AB$

B \ A	0	1
0	1	0
1	1	1

$$\bar{A}\bar{B} + \bar{A}B + AB$$

$$\bar{A}\bar{B} + \bar{A}B$$

$$\bar{A}\bar{B} + AB$$

$$F = \bar{A} + B //$$

③ $F = \bar{A}\bar{B} + AB + \bar{A}B$

B \ A	0	1
0	1	1
1	0	1

$$\bar{A}\bar{B} + AB$$

$$\bar{A}\bar{B} + \bar{A}B$$

$$F = \bar{B} + A //$$

④ $F = \bar{A}BC + ABC + \bar{A}B\bar{C} + \bar{A}B\bar{C}$

C \ AB	00	01	11	10
0	0	1	0	0
1	1	1	1	0

$$= \bar{A}BC + \bar{A}B\bar{C} + ABC$$

$$\bar{A}BC + \bar{A}B\bar{C} + ABC$$

$$= \bar{A}C + \bar{A}B + BC //$$

⑤

A	B	C	F ₁
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

C \ AB	00	01	11	10
0	1	1	1	0
1	0	1	0	1

$$F_1 = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}B\bar{C} + \bar{A}B\bar{C}$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}B\bar{C}$$

$$F_1 = \bar{A}\bar{C} + \bar{A}B + B\bar{C} + A\bar{B}C //$$

$\bar{A}B$ $\bar{A}\bar{B}$ $\bar{A}B$ AB $A\bar{B}$
 $\bar{C}$ 0 1 0 1 0
 C 1 0 1 0 1

$$\bar{A}\bar{B} + \bar{A}\bar{C} + AB + AC$$

⑦ $f = \bar{A}Bc + AC\bar{D} + \bar{C}\bar{D}$

$$\begin{array}{r} \cancel{A} \bar{B} \bar{C} \bar{D} + \bar{A} B \bar{C} \bar{D} + \bar{A} \bar{B} C \bar{D} \\ \cancel{A} \bar{B} C \bar{D} \quad \bar{A} B C \bar{D} \quad A \bar{B} C \bar{D} \\ \cancel{A} B \bar{C} \bar{D} \quad 11 \quad 10 \quad 00 \\ \cancel{A} \bar{B} C \bar{D} \quad 0 \quad 0 \quad 0 \end{array}$$

 $\bar{A}\bar{B} \quad \bar{A}B \quad AB \quad A\bar{B}$

$$F = \bar{C}\bar{D} + \bar{A}BC + A\bar{C}\bar{D}$$

$$⑧ \quad F = \bar{A} + B\bar{C}\bar{D} + A\bar{C}\bar{D} + B\bar{C}D + \bar{A}$$

$$\begin{array}{l} \bar{A}\bar{B}\bar{C}\bar{D} \\ \bar{A}\bar{B}\bar{C}D \\ \bar{A}\bar{B}C\bar{D} \\ \bar{A}\bar{B}CD \\ \bar{A}B\bar{C}\bar{D} \\ \bar{A}B\bar{C}D \\ \bar{A}BC\bar{D} \\ \bar{A}BCD \\ A\bar{B}\bar{C}\bar{D} \\ A\bar{B}\bar{C}D \\ AB\bar{C}\bar{D} \\ AB\bar{C}D \\ ABC\bar{D} \\ ABCD \end{array} + \begin{array}{l} \bar{A}\bar{B}\bar{C}D \\ \bar{A}\bar{B}C\bar{D} \\ \bar{A}\bar{B}CD \\ AB\bar{C}\bar{D} \\ AB\bar{C}D \\ A\bar{B}C\bar{D} \\ ABC\bar{D} \\ ABCD \end{array} + \begin{array}{l} \bar{A}\bar{B}\bar{C}\bar{D} \\ \bar{A}\bar{B}\bar{C}D \\ \bar{A}\bar{B}C\bar{D} \\ \bar{A}\bar{B}CD \\ A\bar{B}\bar{C}\bar{D} \\ A\bar{B}\bar{C}D \\ AB\bar{C}\bar{D} \\ ABC\bar{D} \\ ABCD \end{array}$$

$$= \bar{A} + \bar{B} + A\bar{B}$$

~~$\bar{A} + \bar{C}\bar{D} + \bar{A}\bar{B}$~~

theory - (exam)


Half Adder

(Input 2 bit binary/બાઈનારી 2 bit સંખ્યા)


$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

$$1 + 1 = 2$$

Binary 2002

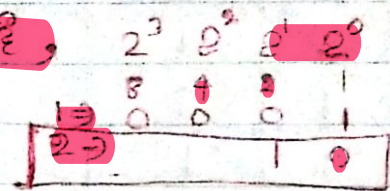

Half adder સંકેત

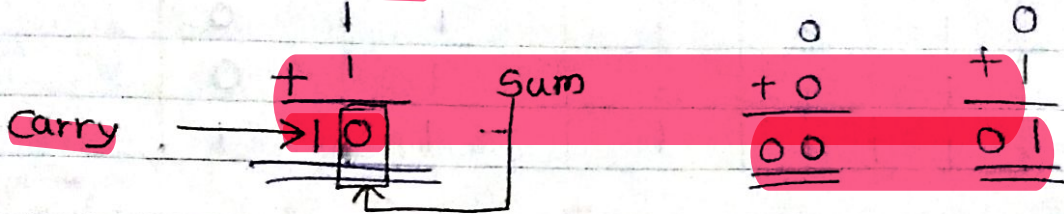


Truth Table :-


A	B	carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

AND

XOR

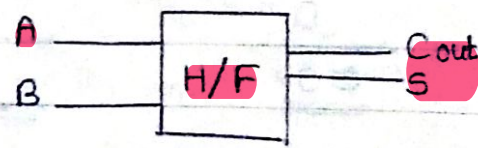

Logic gate for Half Adder.

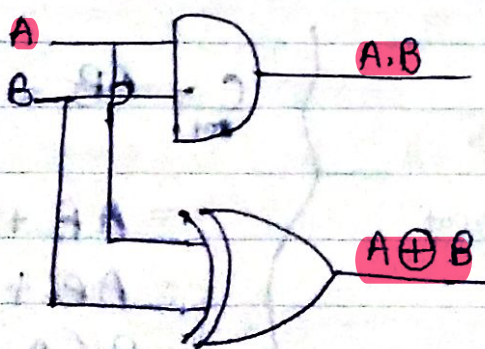

Carry → AND } Half Adder.
Sum → XOR

Full Adder

$(A \cdot B) + (A \cdot C) + (B \cdot C)$
 $A \oplus B \oplus C$

Truth table

A	B	C	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{array}{r}
 \text{Carry} \rightarrow 1 \\
 101 \\
 + 011 \\
 \hline
 001 \\
 \hline
 1001 \leftarrow \text{Sum}
 \end{array}$$

Carry → 0

$$\begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0 \\
 \hline
 00 \leftarrow \text{Sum}
 \end{array}$$

Carry → 0

$$\begin{array}{r}
 0 \\
 + 0 \\
 \hline
 1 \\
 \hline
 1 \leftarrow \text{Sum}
 \end{array}$$

Carry → 1

$$\begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1 \\
 \hline
 0 \leftarrow \text{Sum}
 \end{array}$$

Carry → 1

$$\begin{array}{r}
 1 \\
 + 1 \\
 \hline
 1 \\
 \hline
 1 \leftarrow \text{Sum}
 \end{array}$$


full adder {
 Carry $\rightarrow A \cdot B + B \cdot C + A \cdot C$
 Sum $\rightarrow A \oplus B \oplus C$



$$C = AB + (A \oplus B)C$$

$$\begin{aligned}
 &= AB + (\bar{A}B + A\bar{B})C \\
 &= AB + \bar{A}BC + A\bar{B}C \\
 &= B(A + \bar{A}C) + A\bar{B}C \\
 &= B(A + C) + A\bar{B}C \\
 &= BA + BC + A\bar{B}C \\
 &= A(B + \bar{B}C) + BC \\
 &= A(B + C) + BC \\
 &= AB + AC + BC
 \end{aligned}$$

Full Adder using Half adder

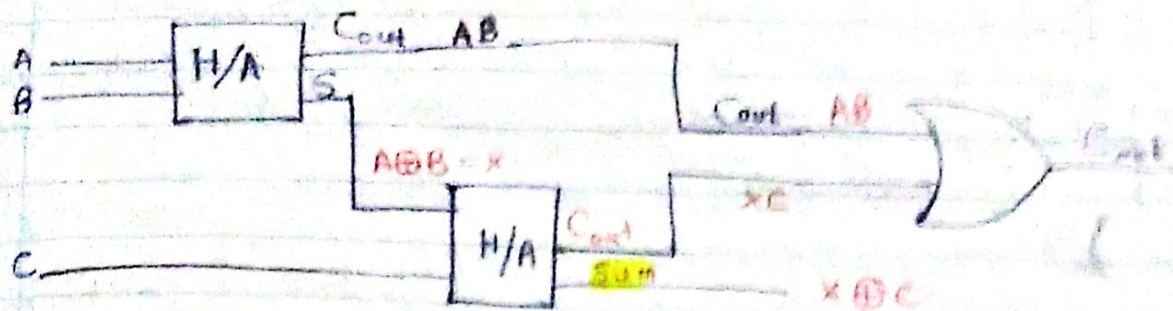

$$\begin{aligned}\text{Sum} &= X \oplus C \\ &= A \oplus B \oplus C\end{aligned}$$

$$\begin{aligned}C_{out} &= AB + XC \\ &= AB + (A \oplus B)C\end{aligned}$$

$$X = A \oplus B$$

$$= A\bar{B} + B\bar{A}$$

$$= A\bar{B} + A\bar{A} + B\bar{A} + B\bar{B}$$

$$= A(\bar{A} + B) + B(\bar{A} + \bar{B})$$


$$X = (\bar{A} + \bar{B})(A + B)$$

$$\begin{aligned}\bar{X} &= \overline{(\bar{A} + \bar{B})(A + B)} \\ X &= \overline{\overline{(\bar{A} + \bar{B})} + \overline{(A + B)}} \\ &= \overline{(\bar{A} + \bar{B})} \cdot \overline{(A + B)}\end{aligned}$$

$$X = \overline{(\bar{A} + \bar{B}) + (A + B)}$$

$$C_{out} = AB$$
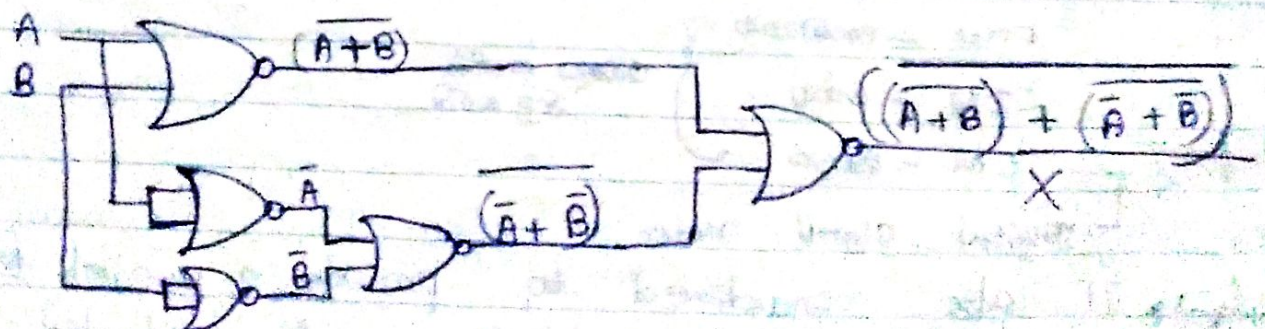
$$\begin{aligned}\overline{C_{out}} &= \overline{AB} \\ &= \bar{A} + \bar{B}\end{aligned}$$





Encoder (D2B)

Decimal to Binary
(Decimal to BCD)


Decimal digit	Binary
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1

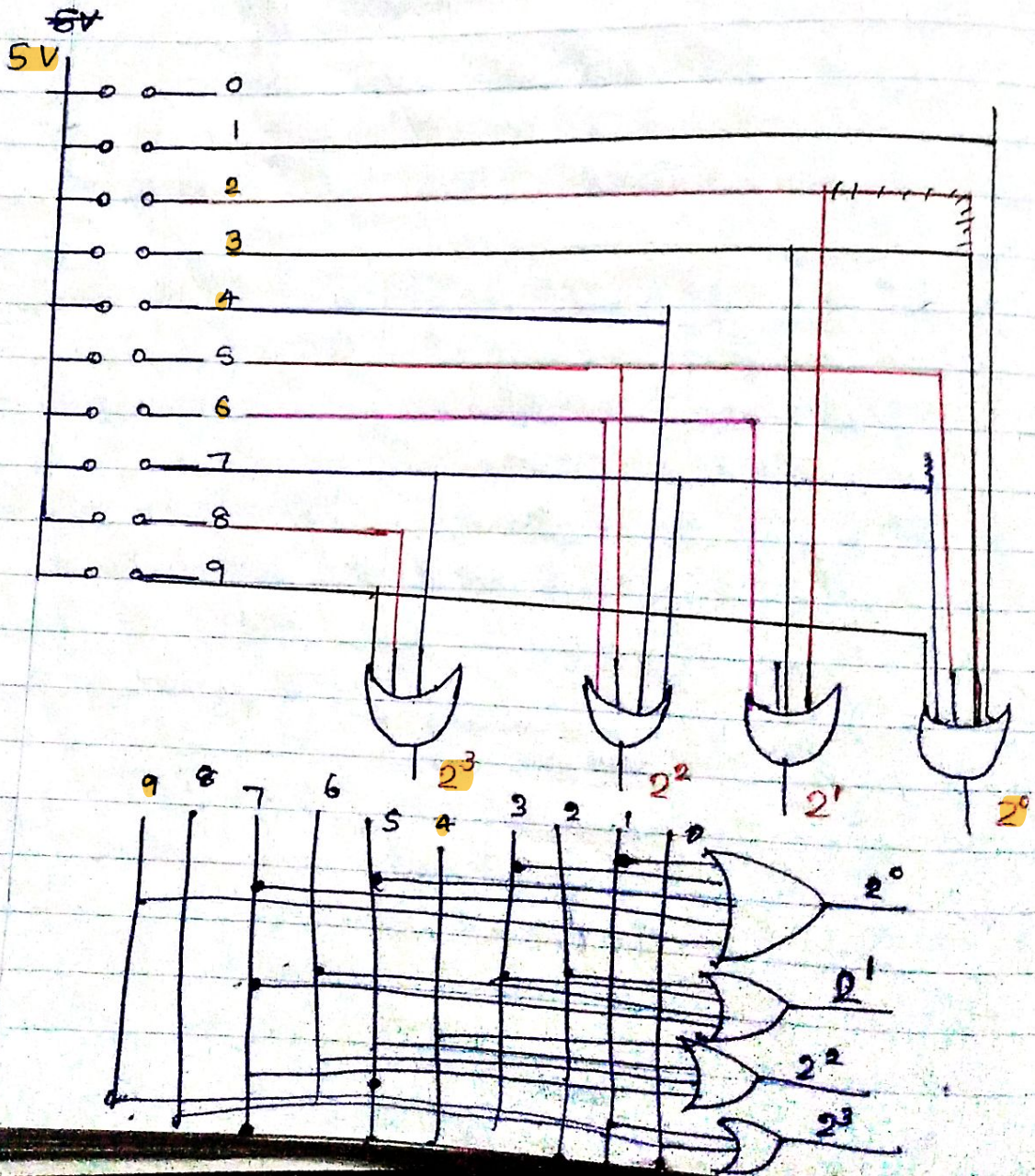Decimal digit
ഉൾപ്പെടെ
binary digit
4 കി ഓക്ക
മെങ്കിലും,
9 കേൾ digit 4
ഉൾപ്പെടെ



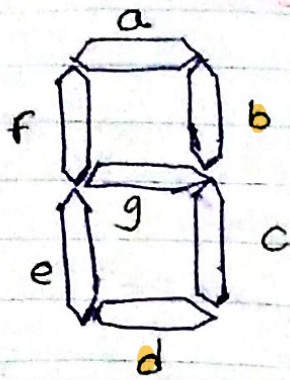

Seven Segment display Decoder

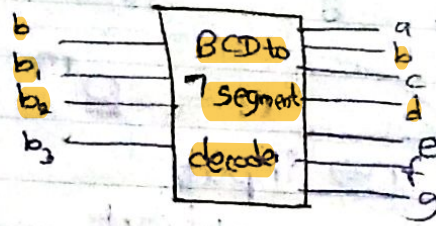

7 segment $\Rightarrow$ create to display

	b_3	b_2	b_1	b_0	a	b	c	d	e	f	g	decimal number
(0)	0	0	0	0	1	1	1	1	1	1	0	0
(1)	0	0	0	1	0	1	1	0	0	0	0	1
(2)	0	0	1	0	1	1	0	1	1	0	0	2
(3)	0	0	1	1	1	1	1	1	0	0	1	3
(4)	0	1	0	0	1	0	1	1	0	1	1	4
(5)	0	1	0	1	1	0	0	1	0	0	1	5
(6)	0	1	1	0	1	0	1	1	1	1	1	6
(7)	0	1	1	1	1	1	1	1	0	0	0	7
(8)	1	0	0	0	1	1	1	1	1	1	1	8
(9)	1	0	0	1	1	1	1	1	1	0	0	9

Multiplexer

* Multiplexer $\rightarrow$ Combinational circuit.

$\hookrightarrow$ is simply a DATA SELECTOR.




Advantages

- ① Reduces no of wires.
- ② Reduces circuit complexity & cost.
- ③ Implementation of various circuits using it.

Decimal to binary Encoder
 * Input 8 and output 3

$n = 2^m$
 n → input
 m → output
 $8 = 2^3$

Input	B_2	B_1	B_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

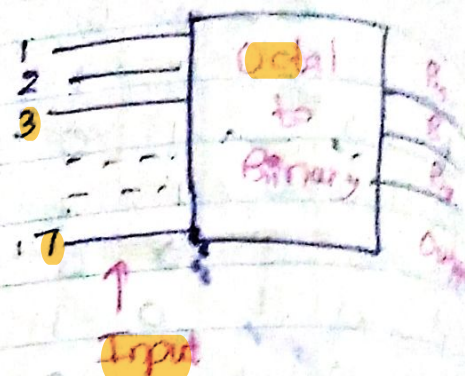


$B_0 \Rightarrow 1 + 3 + 5 + 7$

~~$B_1 \Rightarrow 2 + 3 + 4 + 5 + 6 + 7$~~

$B_1 \Rightarrow 2 + 3 + 6 + 7$

$B_2 \Rightarrow 4 + 5 + 6 + 7$

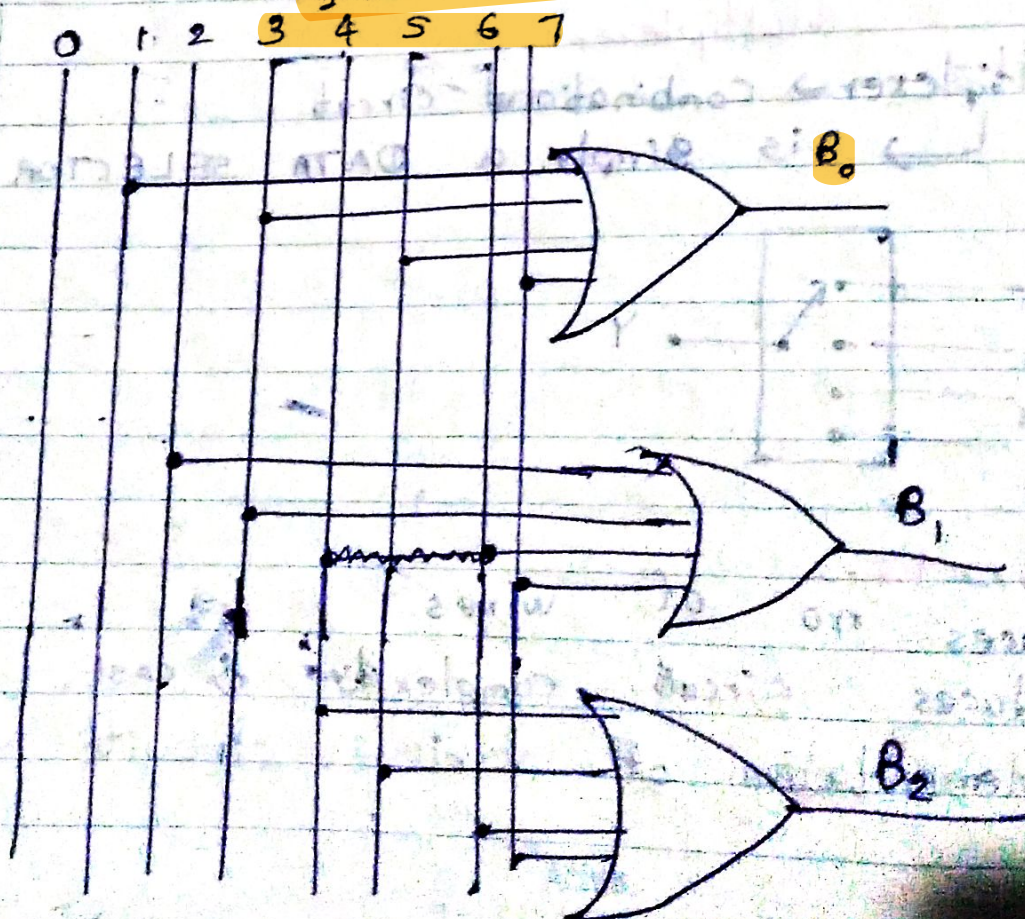

Hexadecimal to binary Decoder. Encoder

$\boxed{16} = 2^4 \leftarrow \text{output}$

Input

Input $B_7 \ B_6 \ B_5 \ B_4 \ B_3$

0 0 0 0 0

1 0 0 0 1

2 0 0 1 0

3 0 0 1 1

4 0 1 0 0

5 0 1 0 1

6 0 1 1 0

7 0 1 1 1

8 1 0 0 0

9 1 0 0 1

A-10 1 0 1 0

B-11 1 0 1 1

C-12 1 1 0 0

D-13 1 1 0 1

E-14 1 1 1 0

F-15 1 1 1 1


16 0 0 0 0



↙ B_0


$$B_0 = 1 + 3 + 5 + 7 + 9 + 11 + 13 + 15.$$
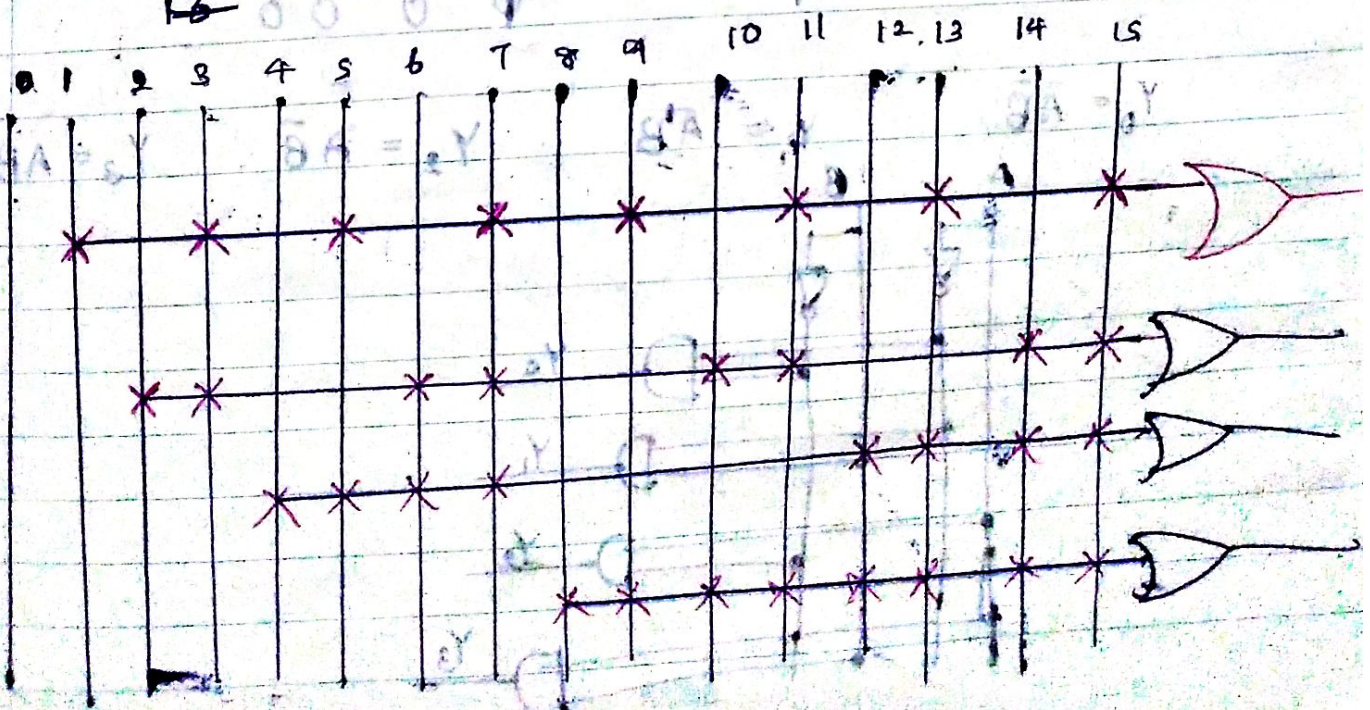
$$B_1 = 2 + 3 + 6 + 7 + 10 + 11 + 14 + 15$$



Decoder
 * Decoder is a multi input circuit which decodes 2^n possible outputs.
 multi output inputs logic into

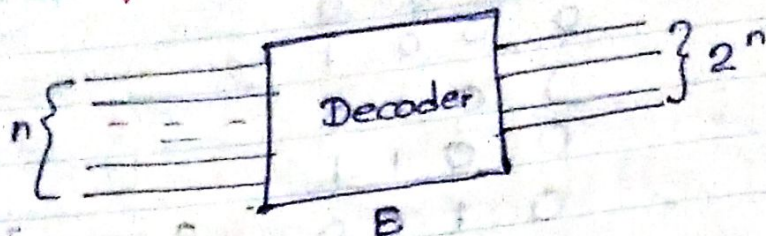* If n = input then $\rightarrow$ Output $\rightarrow 2^n$



Where $\rightarrow E = 0 \rightarrow$ Decoder is disabled
 $\rightarrow E = 1 \rightarrow$ Decoder is enabled.

2 to 4 Decoder


					2^3	2^2	2^1	2^0	
					Y_3	Y_2	Y_1	Y_0	
E	A	B							
0	x	x	0 0	1	0	0	0	0	
1	0	0	1 0	1	0	0	0	1	
	0	1	0 1	1	0	0	1	0	
	1	0	1 1	1	0	1	0	0	
	1	1			1	0	0	0	

$$Y_0 = \bar{A}\bar{B}$$

$$Y_1 = \bar{A}B$$


$$Y_2 = A\bar{B}$$

$$Y_3 = AB$$


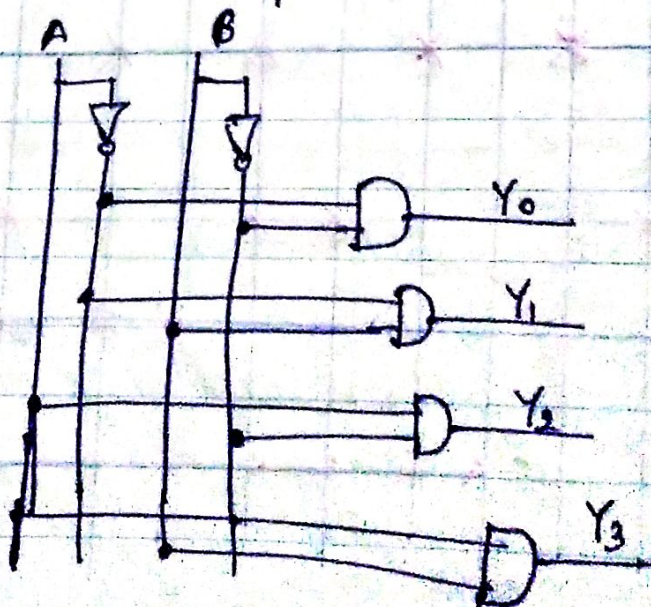


2 to 8 Decoder

	A	B	C		2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0
E	A	B	C		Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
1	0	0	0	$\bar{A}\bar{B}\bar{C}$	0	0	0	0	0	0	0	1
1	0	0	1	$\bar{A}\bar{B}C$	0	0	0	0	0	0	1	0
1	0	1	0	$\bar{A}B\bar{C}$	0	0	0	0	0	1	0	0
1	0	1	1	$\bar{A}BC$	0	0	0	0	1	0	0	0
1	1	0	0	$A\bar{B}\bar{C}$	0	0	0	1	0	0	0	0
1	1	0	1	$A\bar{B}C$	0	0	1	0	0	0	0	0
1	1	1	0	$AB\bar{C}$	0	1	0	0	0	0	0	0
1	1	1	1	ABC	1	0	0	0	0	0	0	0

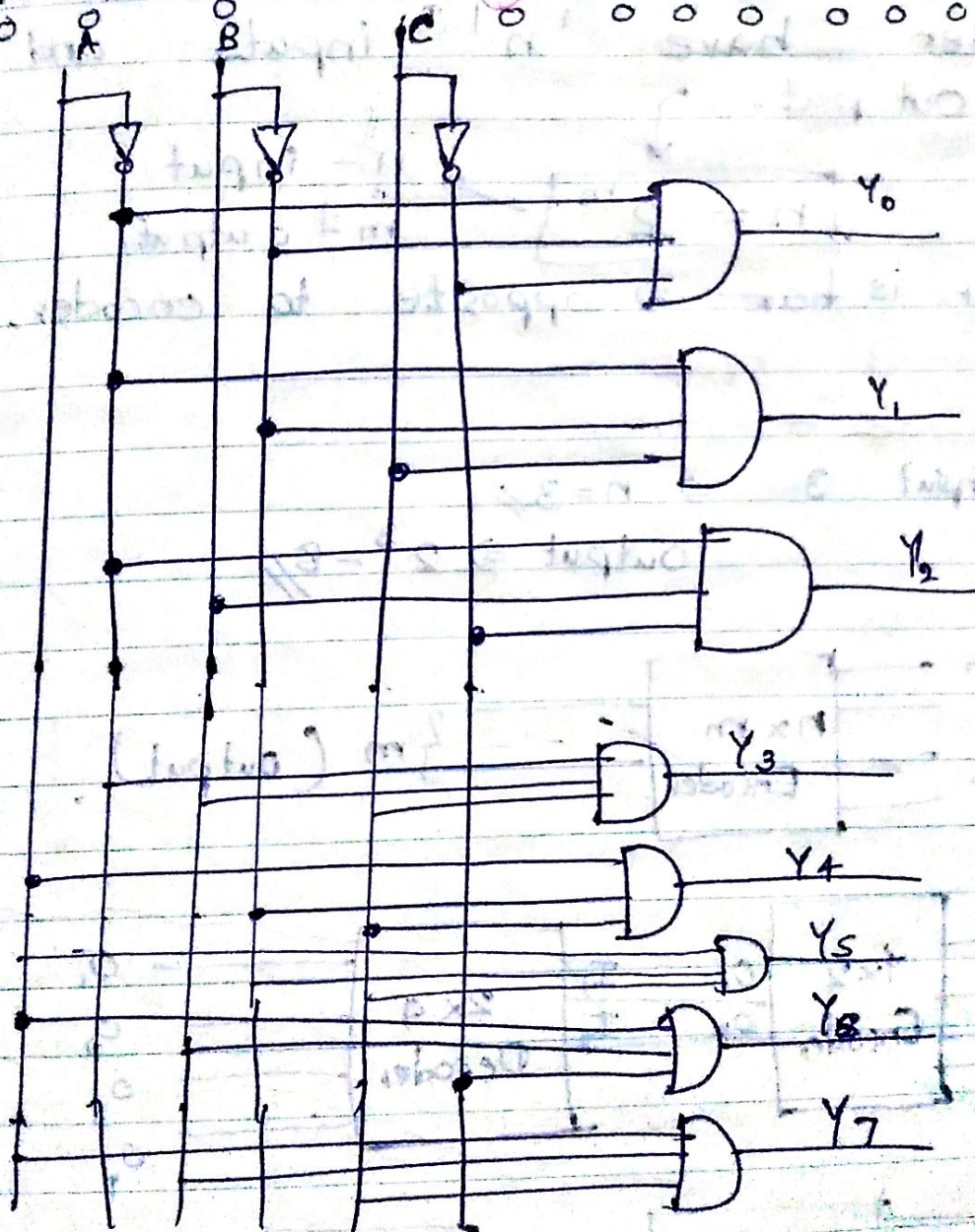


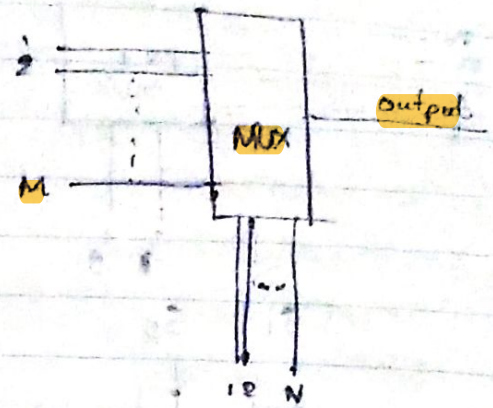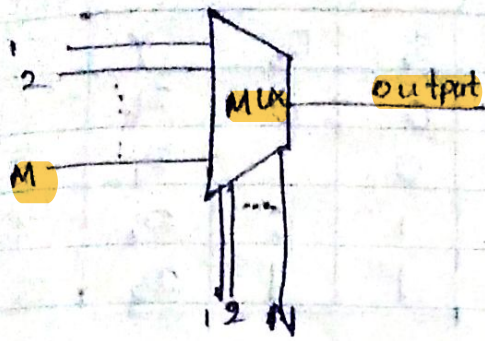Multiplexer $\rightarrow$ Boolean function Implementation




input $M = 2^N \leftarrow$ selection

2x1 MUX

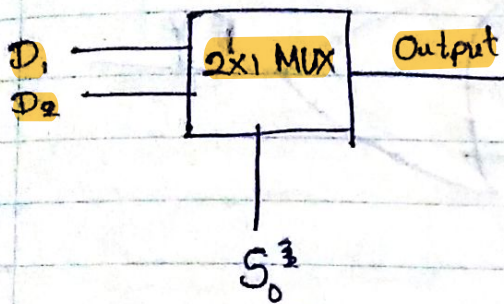


$2 = 2^1$

4x1 MUX

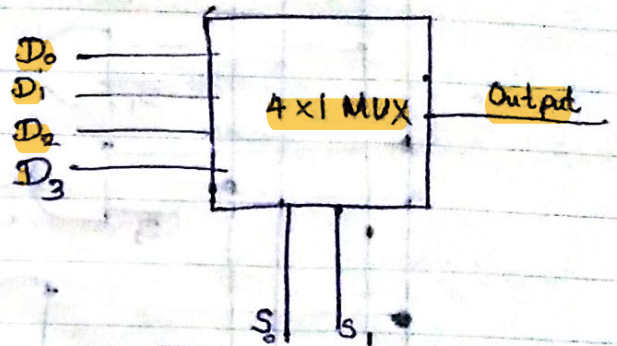

$4 = 2^2$

2x1 Multiplexer

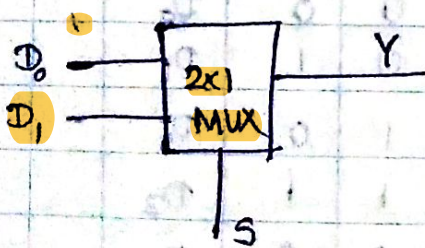

Truth table $\Rightarrow$


S	Y
0	D_0
1	D_1

Circuit


D_0	D_1	S	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_0
0	1	1	D_1
1	0	0	D_0
1	0	1	D_1
1	1	0	D_0
1	1	1	D_1

$Y = S \cdot D_1 + \bar{S} \cdot D_0$

$Y = \bar{S} D_0 + S D_1$

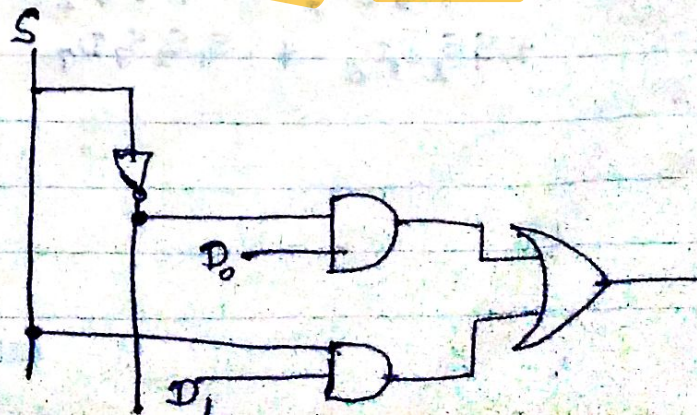

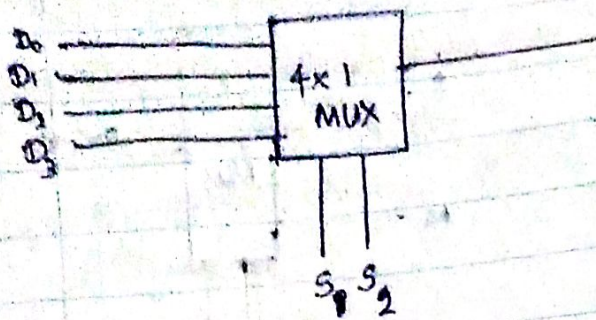
4x1 Multiplexer (Implementation of Boolean Function)




S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$\bar{S}_1 \bar{S}_0 D_0$
 $\bar{S}_1 S_0 D_1$
 $S_1 \bar{S}_0 D_2$
 $S_1 S_0 D_3$
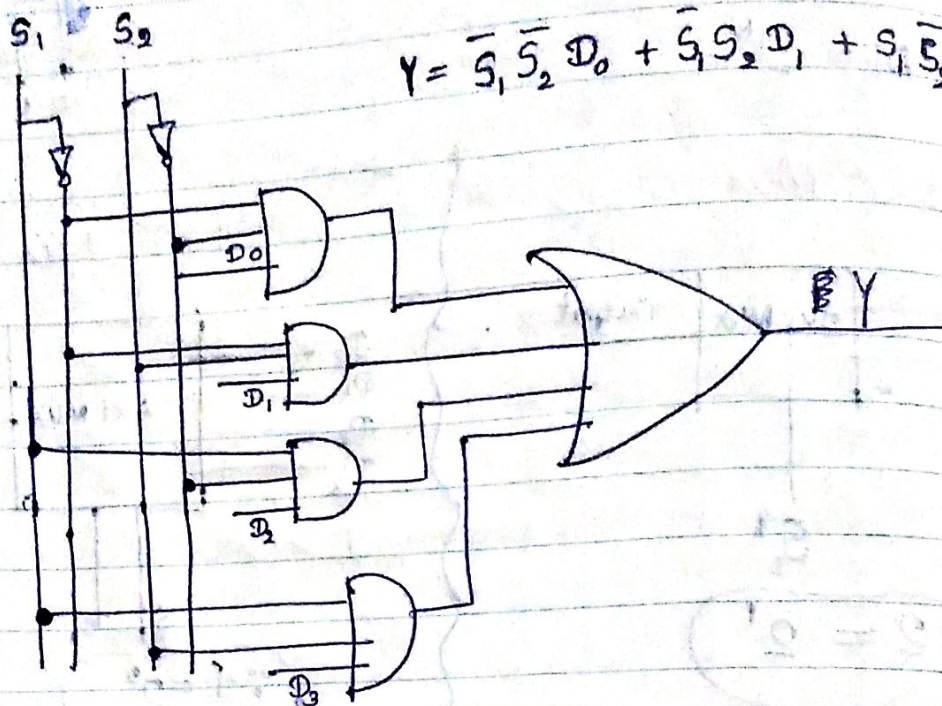
$$Y = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$




8x1 Multiplexer

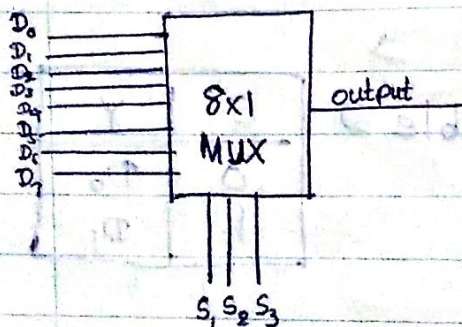


S_1	S_2	S_3	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

$$\begin{aligned}
 Y = & \bar{S}_1 \bar{S}_2 \bar{S}_3 D_0 + \bar{S}_1 \bar{S}_2 S_3 D_1 + \bar{S}_1 S_2 \bar{S}_3 D_2 \\
 & + \bar{S}_1 S_2 S_3 D_3 + S_1 \bar{S}_2 \bar{S}_3 D_4 + S_1 \bar{S}_2 S_3 D_5 \\
 & + S_1 S_2 \bar{S}_3 D_6 + S_1 S_2 S_3 D_7
 \end{aligned}$$

8x1 Multiplexer using 4x1 Multiplexer

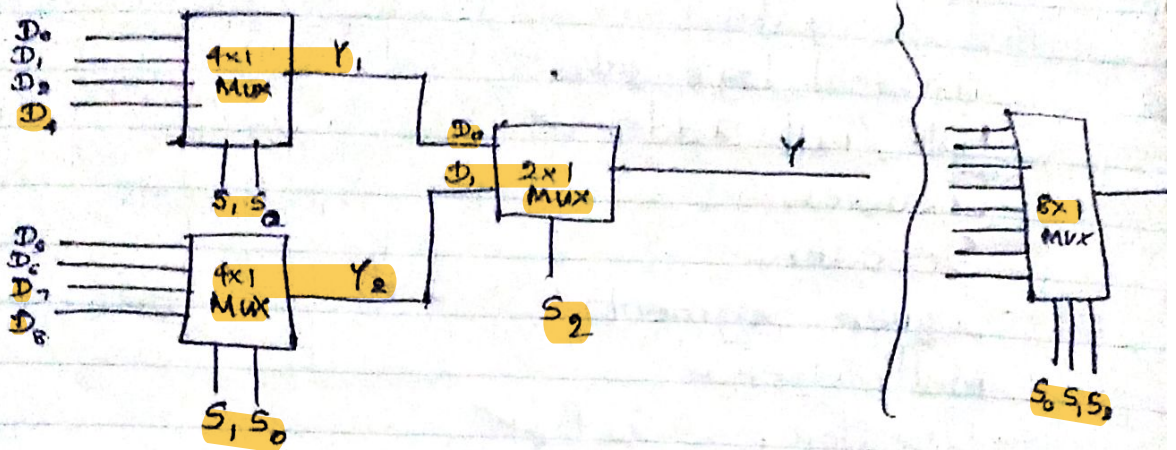

8x1 Multiplexer using 2x1 Multiplexer

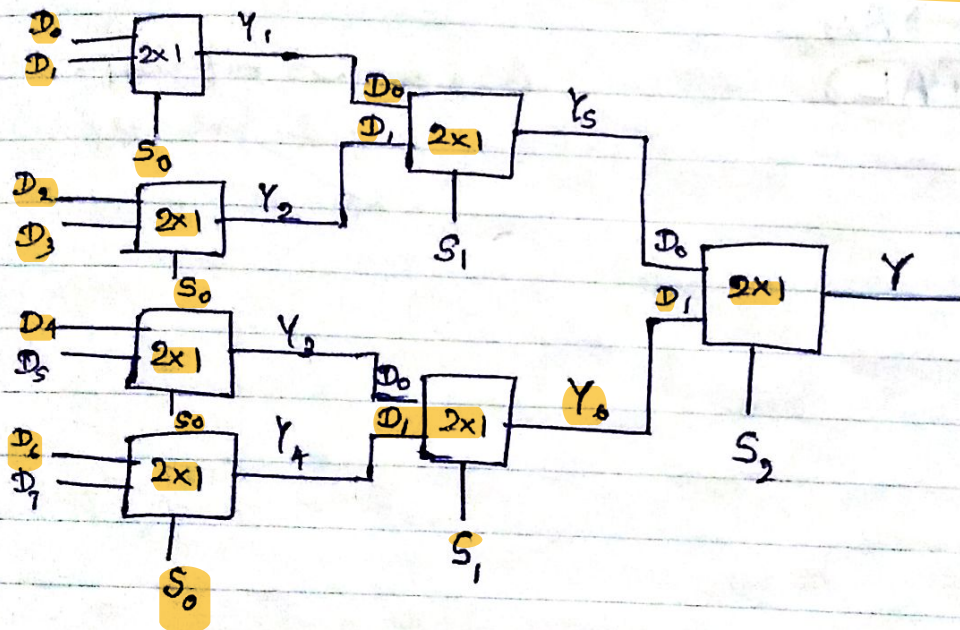

16x1 MUX using 4x1 MUX

